



NUM3 sur owncloud




<https://cloud-soc.lip6.fr/owncloud/public.php?service=files&t=19a15e3a0fff58e8b260c16fc6e54605>

III – Exercice sur l'unité de contrôle







Patrick.Garda@upmc.fr

Control Unit

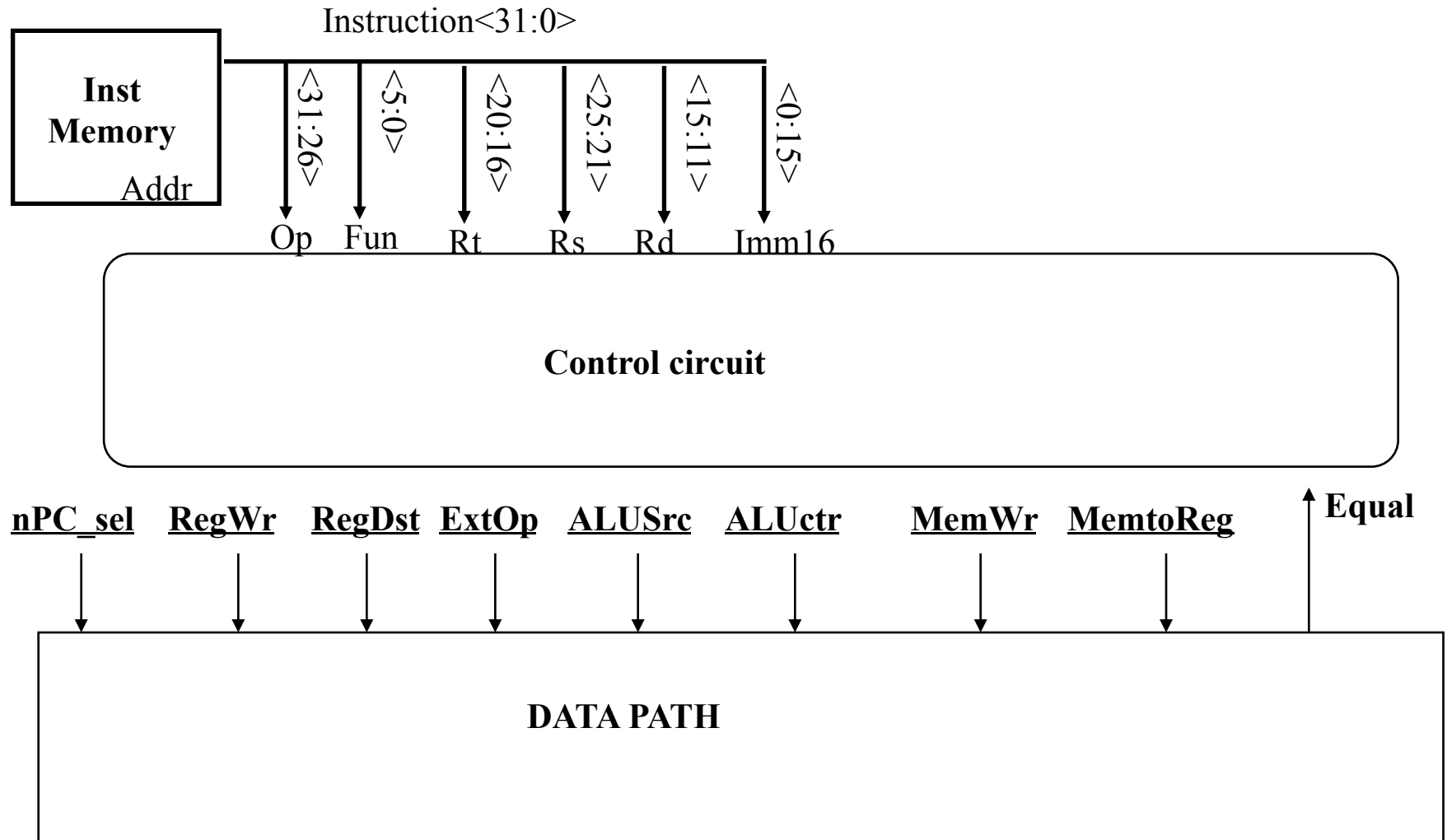

The MIPS-lite Subset

    - add, sub, and, or, slt; e.g.
 - add rd, rs, rt
 - sub rd, rs, rt
- immediate; e.g.
 - ori rt, rs, imm16
- memory reference; e.g.
 - lw rt, rs, imm16
 - sw rt, rs, imm16
- branch:
 - beq rs, rt, imm16






Instruction definition

op | rs | rt | rd | shamt | funct = MEM[PC]

op | rs | rt | Imm16 = MEM[PC]

inst	Register Transfers	
ADD	R[rd] ← R[rs] + R[rt];	PC ← PC + 4
SUB	R[rd] ← R[rs] – R[rt];	PC ← PC + 4
ORI	R[rt] ← R[rs] zero_ext(Imm16);	PC ← PC + 4
LOAD	R[rt] ← MEM[R[rs] + sign_ext(Imm16)];	PC ← PC + 4
STORE	MEM[R[rs] + sign_ext(Imm16)] ← R[rt];	PC ← PC + 4
BEQ	if (R[rs] == R[rt]) PC ← PC + 4 + (SignExt(imm16) x 4) else PC ← PC + 4	

Single Cycle Datapath

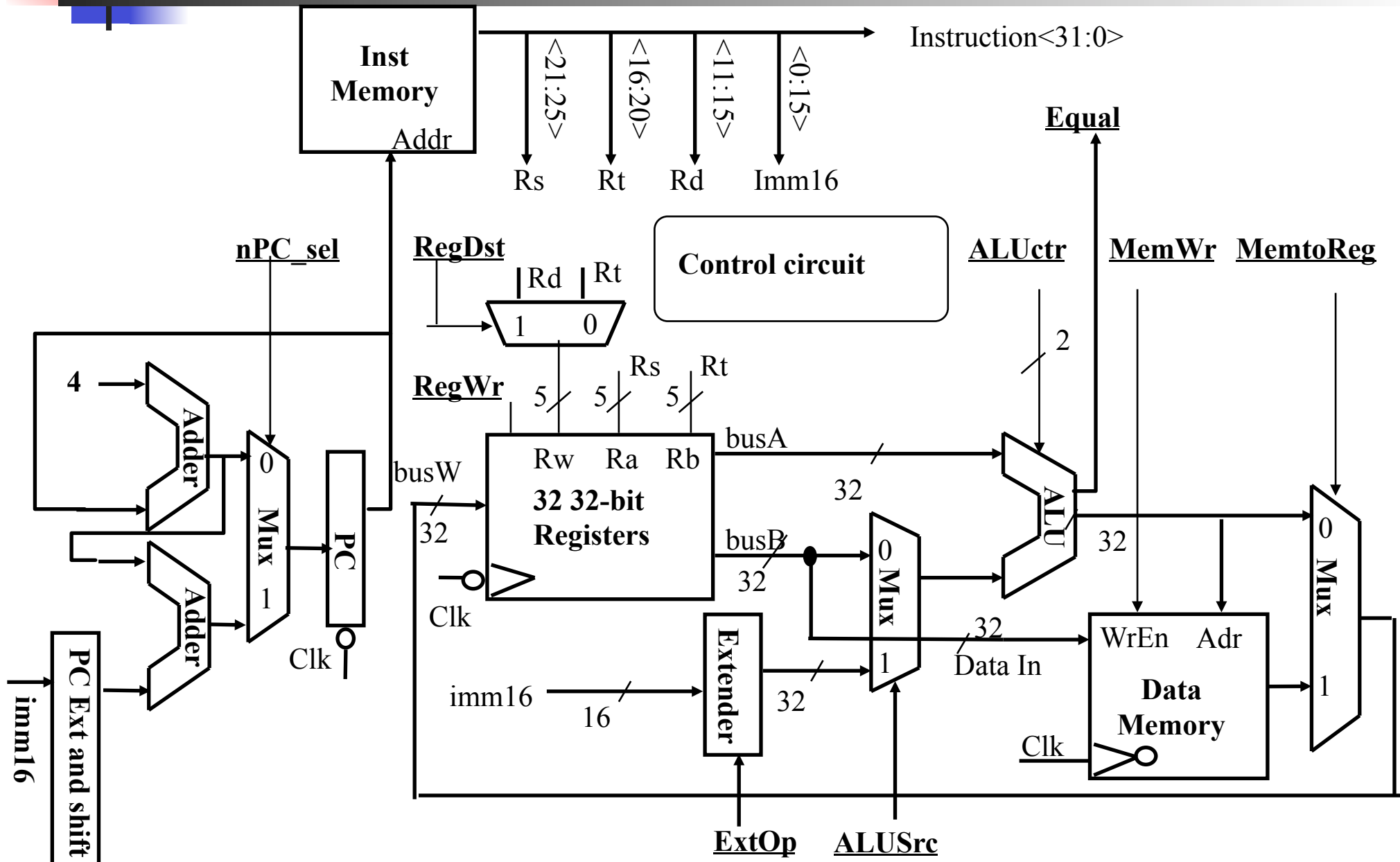

Opcodes and control signal codes

# bit	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
Instruction	OPCODE						rs					rt				?																
ADD	1	1	0	0	0	0	rs					rt				rd				shamt				funct								
SUB	0	1	0	0	0	0	rs					rt				rd				shamt				funct								
ORI	0	0	1	0	0	0	rs					rt				imm16																
LD	0	0	0	1	0	1	rs					rt				imm16																
ST	0	0	0	1	0	0	rs					rt				imm16																
B	0	0	0	0	1	0	rs					rt				imm16																

ALUctr Codes

# bit	A1	A0
ZERO	0	0
ADD	0	1
SUB	1	0
OR	1	1

ExtOp Codes

Unsigned extension	0
Signed extension	1

- MUX codes are given in the block diagram




Control signals

Control signals	« 1 » for instructions:	Boolean expression:
<u>nPC_sel</u>		
<u>RegWr</u>		
<u>RegDst</u>		
<u>ExtOp</u>		
<u>ALUSrc</u>		
<u>ALUctr</u>		
<u>MemWr</u>		
<u>MemtoReg</u>		

IV - Bascules : temps de prépositionnement et de maintien


Patrick.Garda@upmc.fr

Latch D

 

- Si $E = 0$ Latch verrouillé
- Si $E = 1$ Latch transparent

Bascule D

 


■ Si $C = 0$

- Latch Maître transparent
- Latch Esclave verrouillé

■ Si $C = 1$

- Latch Maître verrouillé
- Latch Esclave transparent

Temps prépositionnement

 


- T_{su}
 - Temps prépositionnement
- T_h
 - Temps maintien
- T_{co} T_{c-to-Q} T_p
 - Temps propagation

V - Période du processeur monocycle





Patrick.Garda@upmc.fr

Clocking Methodology

 


- All storage elements are clocked by the same clock edge
- Cycle Time = CLK-to-Q + Longest Delay Path + Setup + Clock Skew
- $(\text{CLK-to-Q} + \text{Shortest Delay Path} - \text{Clock Skew}) > \text{Hold Time}$

Register-Register Timing

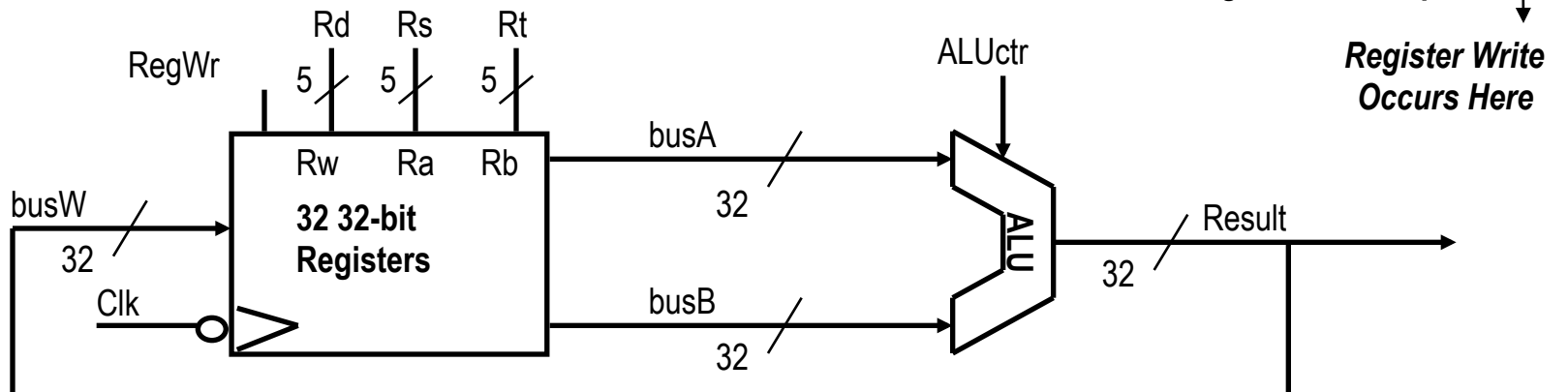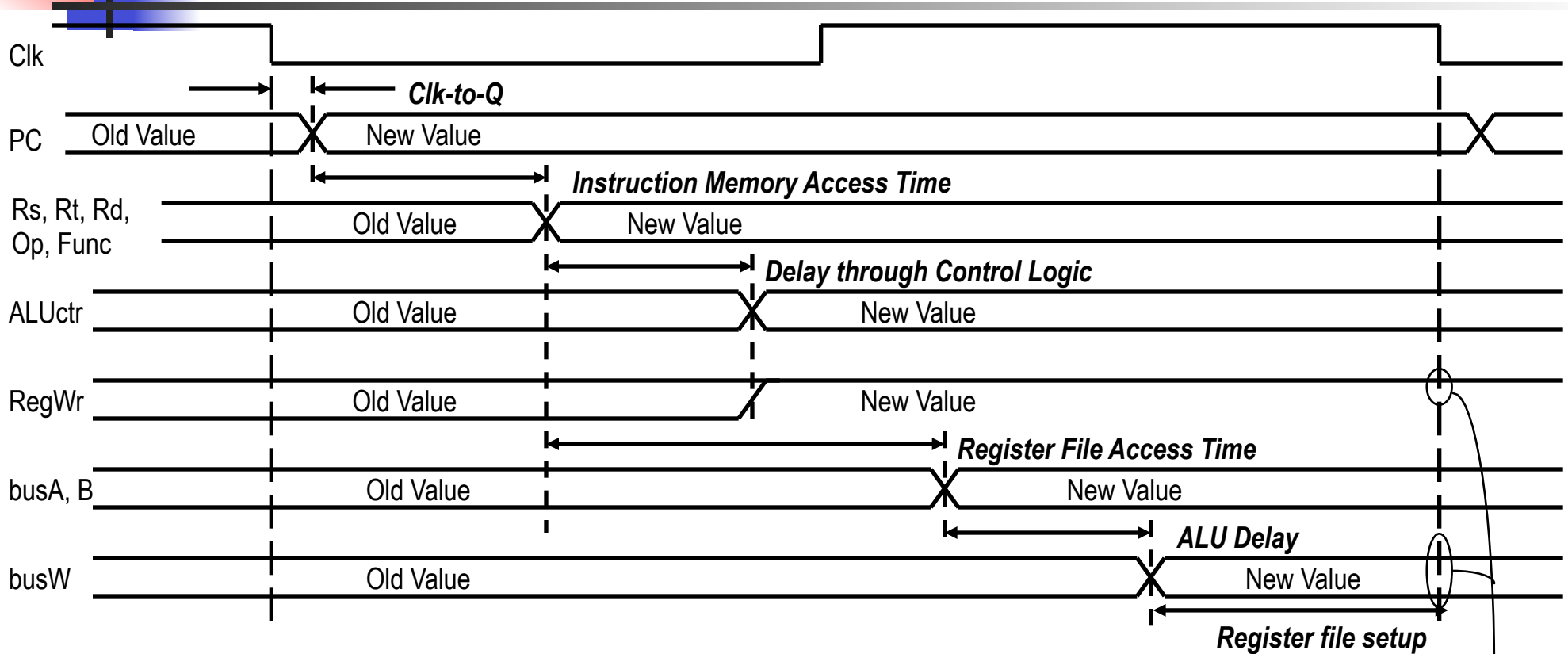

Worst Case Timing (Load instruction)

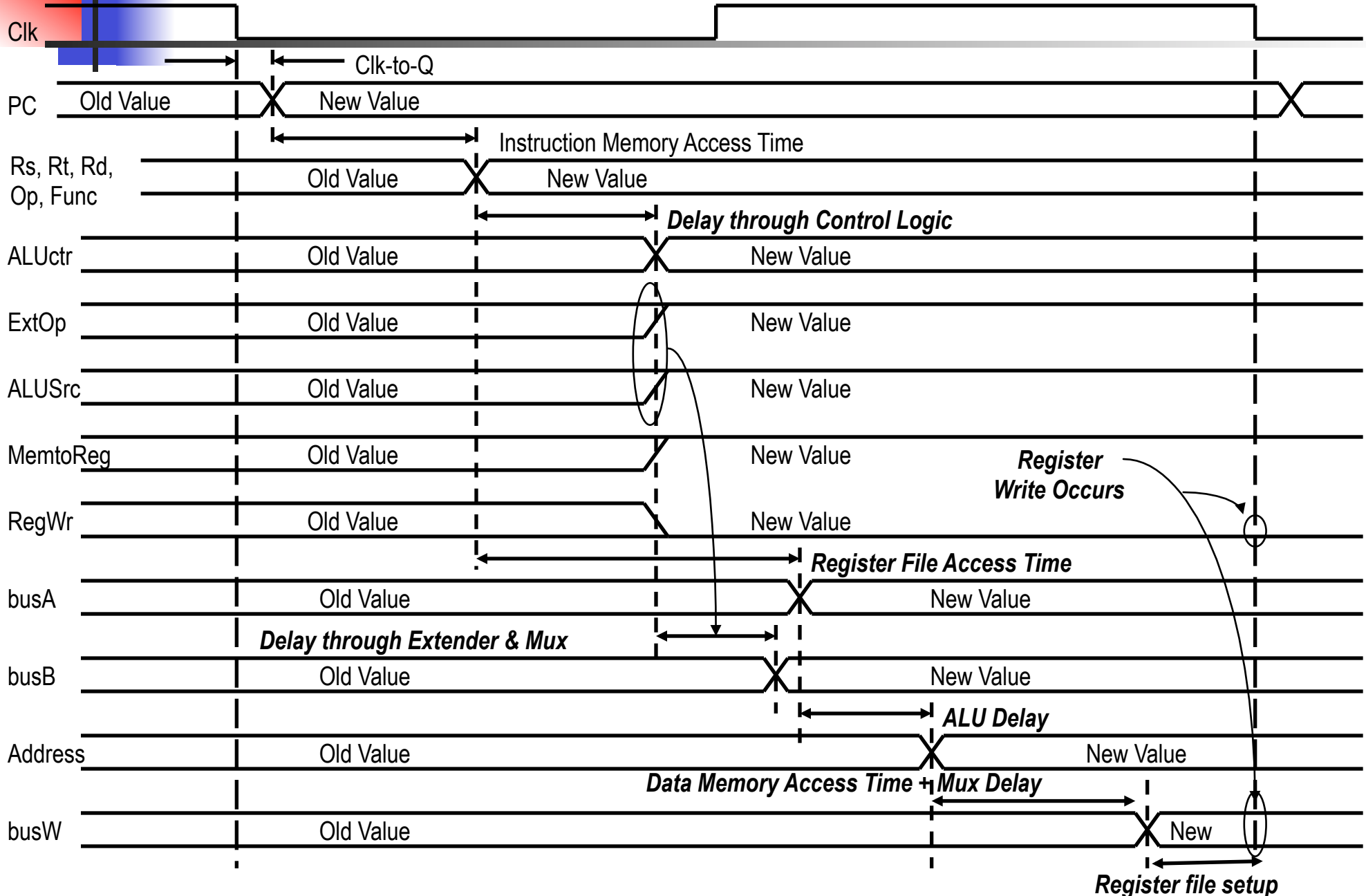

What is the minimum clock period?


ADD and SUB



ORI



Load

 

← Critical Path →

Store




BEQ





Library Timing Data

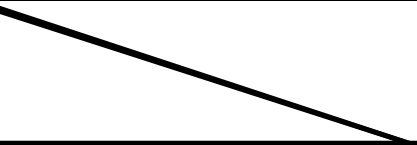	ALU/Adder	Extender	MUX	Control circuit	Register file PC	Memory
Propagation time	20 ns	10 ns	10 ns	20 ns	10 ns	20 ns
Setup time					10 ns	10 ns
Hold time					0 ns	0 ns



■ **Units:**

[illegible]

- **Timing:**

[illegible]